

# Vježbe F,

## STRUJNI KRUGOVI

jakost struje  $I = \frac{\Delta Q}{\Delta t}$

Ohmov zakon  $U = R \cdot I$   $I = \frac{U}{R}$


Snaga  $P = U \cdot I = I^2 R = \frac{U^2}{R}$

otpor i otpornost  $R = \rho \cdot \frac{l}{S}$

provodnost (vodljivost)  $\sigma = \frac{1}{\rho}$  ( $\Omega^{-1} m^{-1}$ )

gustoća struje  $\vec{j} = \sigma \vec{E}$ ,  $j = \frac{I}{S}$

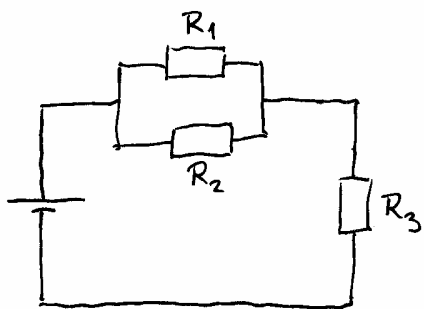- 25) Kroz otpornik  $R_2$  na shemi teče struja 0.4 A. Odredite napon izvora, snagu koju troši svaki od tri otpornika i ukupnu snagu u strujnom krugu.  $R_1 = 1 \Omega$ ,  $R_2 = 2 \Omega$ ,  $R_3 = 3 \Omega$ .



$$U_2 = I_2 R_2 = 0.8 \text{ V}$$

$$I_1 = \frac{U_2}{R_1} = 0.8 \text{ A}$$

$$I_3 = I_1 + I_2 = 1.2 \text{ A}$$

$$U_3 = I_3 R_3 = 3.6 \text{ V}$$

$$U = U_2 + U_3 = 4.4 \text{ V}$$


$$P_1 = I_1 U_1 = 0.64 \text{ W}$$

$$P_2 = I_2 U_2 = 0.32 \text{ W}$$

$$P_3 = I_3 U_3 = 4.32 \text{ W}$$

$$P = P_1 + P_2 + P_3 = U \cdot I_3 = 5.28 \text{ W}$$

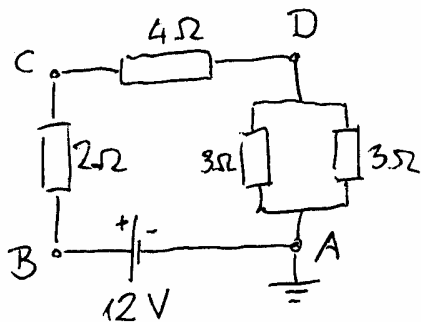- 26) U strujnom krugu na slici odredite potencijale točaka ABCD i napon između B i D



$$R_{\text{uk}} = 2 \Omega + 4 \Omega + 1.5 \Omega = 7.5 \Omega$$

$$I = \frac{U}{R} = \frac{12}{7.5} = 1.6 \text{ A}$$

$$V_A = 0$$


$$V_B = 12 \text{ V}$$

$$V_C = 8.8 \text{ V}$$

$$V_D = 2.4 \text{ V}$$

$$U_{BD} = 9.6 \text{ V}$$

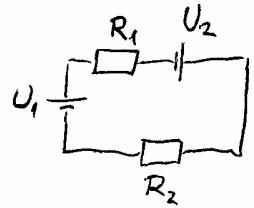- 27) Napon izvora  $U_2$  na shemi je 65% viši od napona  $U_1$ . Odredite oba napona ako je ukupna snaga na otpornicima 17W.  $R_1 = 10\Omega$ ,  $R_2 = 15\Omega$



$$P = U \cdot I = I^2 R, \quad R = R_1 + R_2 = 25\Omega$$


$$17 = I^2 \cdot 25, \quad I = \sqrt{0.68} = 0.82462 \text{ A}$$

$$U = I \cdot R = 20.6155 \text{ V} = 2.65 U_1$$

$$U_1 = 7.7794 \text{ V}$$

$$U_2 = 12.8361 \text{ V}$$

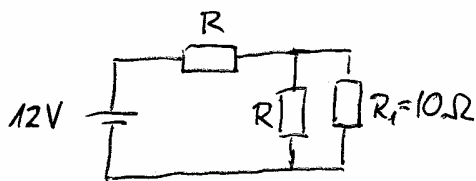- 28) Odredite otpor  $R$  (dva otpornika na shemi) ako kroz otpornik  $R_1$  teče struja 0.5A



$$U_1 = R_1 I_1 = 10 \cdot 0.5 = 5 \text{ V}$$

$$U_2 = U_1 = 5 \text{ V}$$

$$U_3 = 12 \text{ V} - U_1 = 7 \text{ V}$$

$$R = \frac{7 \text{ V}}{I} = \frac{5 \text{ V}}{I - 0.5 \text{ A}}$$

$$\begin{aligned} 7I - 3.5 &= 5I \\ 2I &= 3.5 \\ I &= 1.75 \text{ A} \end{aligned} \quad \Rightarrow \quad R = \frac{7 \text{ V}}{1.75 \text{ A}} = \frac{5 \text{ V}}{1.25 \text{ A}} = 4 \Omega$$

- 29) Odredite ukupan otpor sklopa otpornika na slici

$$R_1 = 10 \Omega$$

$$R_2 = 14 \Omega$$

$$R_3 = 3.75 \Omega$$

$$R_4 = 3.25 \Omega$$

$$R_5 = 2 \Omega$$

$$R_6 = 9 \Omega$$

$$R_{34} = R_3 + R_4 = 7 \Omega$$


$$R_{234} = \frac{R_2 \cdot R_{34}}{R_2 + R_{34}} = \frac{14 \cdot 7}{14 + 7} = \frac{14}{3} \Omega$$

$$R_{2345} = R_5 + R_{234} = \frac{14}{3} \Omega + \frac{6}{3} \Omega = \frac{20}{3} \Omega$$

$$\frac{1}{R_{15}} = \frac{1}{R_1} + \frac{1}{R_{25}} = \frac{1}{10} + \frac{3}{20} = \frac{5}{20} \Omega^{-1}$$

$$R_{15} = 4 \Omega$$
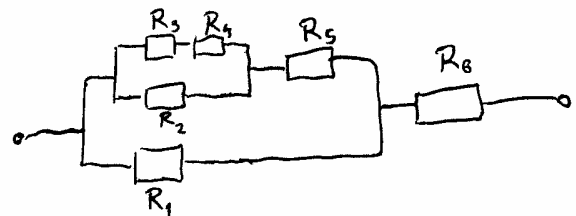
$$R_{\text{UK}} = R_{15} + R_6 = 4 \Omega + 9 \Omega = 13 \Omega$$




- 30) Odredite potencijale točaka ABC i D na shemi.  
Kolika struja teče kroz otpornik  $R_3$ ?

$$U = 18.18V$$

$$R_1 = R_2 = 14.4\Omega$$

$$R_3 = R_4 = 18\Omega$$

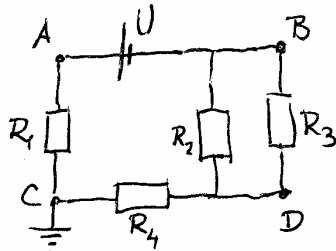

$$R_{UK} = R_1 + R_4 + \frac{R_2 R_3}{R_2 + R_3} = 14.4 + 18 + \frac{14.4 \cdot 18}{14.4 + 18} = 40.4\Omega$$

$$I = \frac{U}{R_{UK}} = \frac{18.18V}{40.4\Omega} = 0.45A$$

potencijali:  $U_C = 0V$  (uzemljeno)


$$U_A = U_C + U_{R1} = 0 + 0.45 \cdot 14.4 = 6.48V$$

$$U_B = U_A - U = -11.7V = 6.48 - 18.18$$

$$U_D = U_C - U_{R4} = 0 - 0.45 \cdot 18 = -8.1V$$

$$I_3 = \frac{U_3}{R_3} = \frac{U_D - U_B}{R_3} = \frac{-8.1 + 11.7}{18} = 0.2A$$

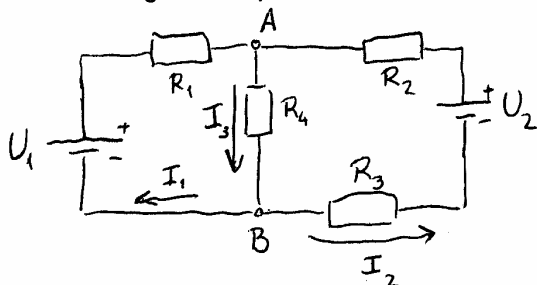- 31) Odredite jakost električnih struja u granama mreže na slici.  
Koliki je napon  $U_{AB}$ ?



$$U_1 = 4V$$

$$U_2 = 6V$$

$$R_1 = 1\Omega$$

$$R_2 = 2\Omega$$

$$R_3 = 4\Omega$$

$$R_4 = 4\Omega$$

Kirchoffovi zakoni

$$U_1 = I_1 R_1 + I_3 R_4$$

$$U_2 = I_2 (R_2 + R_3) + I_3 R_4$$

$$I_3 = I_1 + I_2$$

$$4 = 1I_1 + 4(I_1 + I_2)$$

$$6 = 6I_2 + 4(I_1 + I_2)$$

$$4 = 5I_1 + 4I_2 \quad | \cdot 5$$

$$6 = 4I_1 + 10I_2 \quad | \cdot (-2)$$

$$20 = 25I_1 + 20I_2$$

$$-12 = -8I_1 - 20I_2$$

$$8 = 17I_1$$


$$I_1 = \frac{8}{17} = 0.47A$$

$$I_2 = 1 - \frac{5}{4}I_1 = 1 - \frac{5}{4} \cdot \frac{8}{17} = \frac{7}{17} = 0.41A$$

$$I_3 = \frac{15}{17} = 0.88A$$

$$U_{AB} = I_3 R_4 = \frac{60}{17} = 3.53V$$

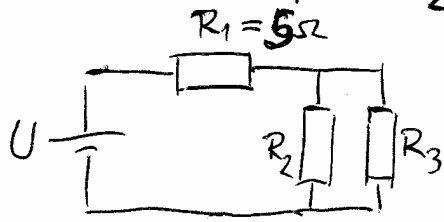- 32) Na otporniku  $R_3 = 10\Omega$  napon iznosi 64% napona izvora, a jouleova toplina ima snagu 6.4W. Odredite napon izvora, struju kroz  $R_1$  i ukupnu snagu koju traži strujni krug. Koliki je otpor  $R_2$ ?



$$P = U \cdot I_1 = 11.25 \text{ W}$$

$$P_3 = U_3 I_3 = \frac{U_3^2}{R_3}$$

$$I_1 = 0.9 \text{ A}$$

$$U_3 = \sqrt{P_3 R_3} = 8 \text{ V}$$

$$I_3 = 0.8 \text{ A}$$

$$U = \frac{U_3}{0.64} = 12.5 \text{ V}$$

$$I_2 = I_1 - I_3 = 0.1 \text{ A}$$


$$U_1 = U - U_3 = 4.5 \text{ V}$$

$$R_2 = \frac{U_3}{I_2} = \frac{8}{0.1} = 80 \Omega$$

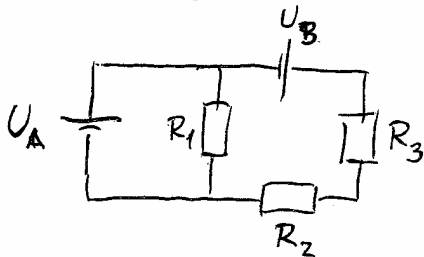- 33) (3/9.6.2017.)

Odredite struju kroz  $R_2$  i napon na  $R_2$  na shemi.

$$U_A = 7 \text{ V}, U_B = 14 \text{ V}, R_1 = 7 \Omega, R_2 = 7 \Omega, R_3 = 8 \Omega$$



$$U_1 = U_A = 7 \text{ V}, I_1 = \frac{U_1}{R_1} = 1 \text{ A}$$

$$U_2 + U_3 = I_2 (R_2 + R_3) = 14 + 7 = 21 \text{ V}$$

$$I_2 = \frac{21}{15} = 1.4 \text{ A}$$

$$U_2 = I_2 R_2 = 9.8 \text{ V}$$

- struktura atoma, jezgra
- radioaktivnost (raspadi) i nukl. reakcije (nastanak svih jezgri, stabilnih i radioaktivnih)
- izotopi (~ 1930, nakon otkrića neutrona)
- statistički karakter raspada: idealan sat, atomi ne stare  
atomima su identični
- defekt mase, E vezanja

$$N = N_0 \cdot 2^{-\frac{t}{T}}$$

|  
br. at. u t=0  
broj atoma nakon t

vrijeme poluraspada

$$2^x = e^{(\ln 2)x} = e^{x \ln 2}$$

$$\frac{dN}{dt} = N_0 \cdot 2^{-\frac{t}{T}} \cdot \frac{-\ln 2}{T} = -\frac{N}{T} \ln 2$$

$$A = \left| \frac{dN}{dt} \right|, [A] = \text{Bq (bekerel, raspad u sekundi)}$$

34) Odredite atomsku težinu magnezija iz učestalosti i masa izotopa:

24 Mg	78.99%	23.98504	
25 Mg	10.00%	24.98584	
26 Mg	11.01%	25.98260	
24.3202		24.30505	(tbl. 24.305)

35) Odredite udjele dvaju prirodnih izotopa klora,  $^{35}\text{Cl}$ ;  $^{37}\text{Cl}$ , ako je atomska masa 35.453

približno:  $35.453 = p \cdot 35 + (1-p) \cdot 37$   
 $\Rightarrow p = 77.35\% \text{ } ^{35}\text{Cl}$   
 $22.65\% \text{ } ^{37}\text{Cl}$

točnije

$$35.453 = p \cdot 34.96885 + (1-p) \cdot 36.96950$$

$$1.5165 = p \cdot 2.00065 \quad \begin{array}{l} 75.80\% \text{ } ^{35} \\ 24.20\% \text{ } ^{37} \end{array}$$

36) Koliki se postotak  $^{14}\text{C}$  raspadne 1000 godina nakon nastanka?

$$T = 5730 \text{ Y}$$

$$\frac{N}{N_0} = 2^{-\frac{1000}{5730}} = 0.886$$

88.6% ostane  $^{14}\text{C}$   
 11.4% se raspadne u  $^{14}\text{N}$

37) Odredite masu i množinu radioaktivnog izvora  $^{241}\text{Am}$ , aktivnosti 70 kBq.  $T = 432.2\text{Y}$

$$70\ 000 = \frac{N \ln 2}{432.2 \cdot 365.25 \cdot 24 \cdot 3600} \Rightarrow N = 1.3774 \cdot 10^{15} \text{ atoma}$$

$$n = \frac{N}{N_A} = 2.2873 \cdot 10^{-9} \text{ mol}, \quad m = nM = 5.51 \cdot 10^{-7} \text{ g} = 0.551 \mu\text{g}$$

b) Kolika će biti aktivnost nakon 30 godina?

$$A = A_0 \cdot 2^{-\frac{t}{T}} = 70 \text{ kBq} \cdot 2^{-\frac{30}{432.2}} = 66.71 \text{ kBq}$$

c) Kolika nakon 3000 godina?

$$A = 70\ 000 \cdot 2^{-\frac{3000}{432.2}} = 570 \text{ Bq}$$